

13.2 Band-Stop Filter

Figure 12 shows an example of an analog bandstop filter.

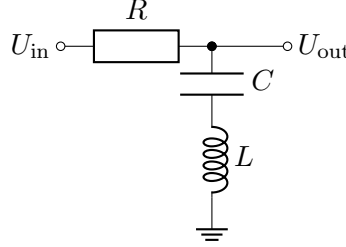


Figure 12: A simple analog bandstop filter.

To analyze the filter, we first define an equivalent circuit in which the series CL branch is replaced by an element with impedance

$$Z_{\text{eq}} = Z_C + Z_L = \frac{1}{i\omega C} + i\omega L = \frac{1}{sC} + sL = \frac{1 + s^2 LC}{sC},$$

where we have replaced $i\omega$ with the Laplace-domain frequency s . We then write the voltage drop equations

$$U_{\text{in}} - U_{\text{out}} = IR \quad \text{and} \quad U_{\text{out}} = IZ_{\text{eq}}$$

and then equate currents to get

$$U_{\text{in}} - U_{\text{out}} = \frac{R}{Z_{\text{eq}}} U_{\text{out}} \implies H = \frac{U_{\text{out}}}{U_{\text{in}}} = \frac{Z_{\text{eq}}}{R + Z_{\text{eq}}}.$$

After substituting in the equivalent impedance, the filter's transfer function is

$$H(s) = \frac{1 + s^2 LC}{sRC + 1 + s^2 LC}.$$

We then divide numerator and denominator by LC to get the standard expression

$$H(s) = \frac{s^2 + (1/LC)}{s^2 + (R/L) \cdot s + 1/(LC)} \equiv \frac{s^2 + \omega_0^2}{s^2 + s\omega_c + \omega_0^2},$$

where we have defined the parameters $\omega_c = R/L$ and $\omega_0^2 = 1/(LC)$.

Following an analogous procedure to the bandpass filter analysis in the previous exercise, we find that the bandstop filter's frequency width at -3 dB attenuation is

$$\Delta\omega_{-3\text{ dB}} = \omega_c = \frac{R}{L}.$$

The circuit's quality factor is

$$Q \equiv \frac{\omega_0}{\Delta\omega_{-3\text{ dB}}} = \frac{\omega_0}{\omega_c} = \frac{L}{R} \frac{1}{\sqrt{LC}}.$$